



Course Name:	Elements of Electrical and Electronics Engineering	Semester:	I
Date of Performance:	22 / 11 / 2022	Batch No:	C2-2
Faculty Name:	Jyoti Varavedkar	Roll No:	16010122109
Faculty Sign & Date:		Grade/Marks:	/ 25

Experiment No: 5

Title: Maximum Power Transfer Theorem

Aim and Objective of the Experiment:


- To observe maximum power transfer in D.C. circuit.

COs to be achieved:

CO1: Analyze resistive networks excited by DC sources using various network theorems.

Circuit Diagram/ Block Diagram:

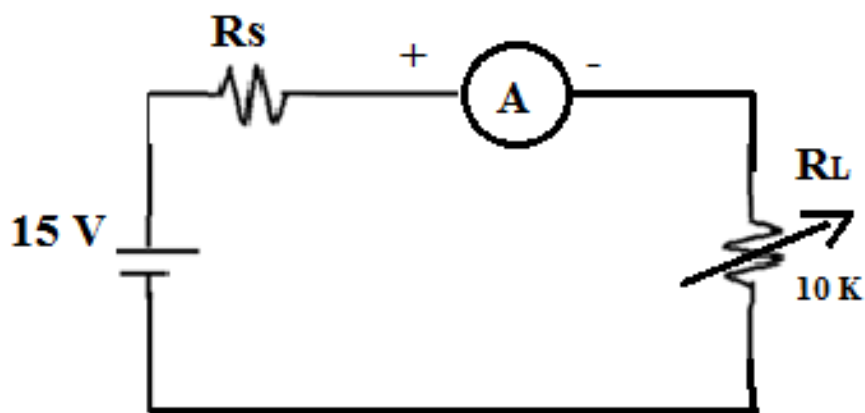Circuit Diagram: $V_s = 50 \text{ V}$ and $R_s = 500 \Omega$



Stepwise-Procedure:

1. Set D.C. supply voltage $V = 15\text{ V}$.
2. Vary R_L in the range $50\ \Omega$ - $10\text{ K}\Omega$ in steps of $100\ \Omega$.
3. Note down I_L and V_L for each value of R_L . Where I_L and V_L are current through R_L and voltage across R_L respectively.
4. Prepare observation table showing readings of R_L Vs power $P := I_L \cdot V_L$
5. Plot graph of P Vs R_L
6. Locate the point of maximum value of power P and note down corresponding value of R_L .
. Verify the results theoretically


Observation Table: $R_{th} = 815\ \Omega$



Sr No	$R_L \Omega$	Circuit Current (I_L) mA		Power absorbed by load (P_L) W $P_L = I^2 \cdot R_L$	
		Th	Pr	Th ($\times 10^4$)	Pr ($\times 10^4$)
1.	238	14.78	14.68	5.2	4.6
2.	365	12.66	12.85	5.8	6.2
3.	557	10.89	11.08	6.6	6.6
4.	700	9.87	9.80	6.81	6.8
5.	815	9.17	9.25	6.85	6.9
6.	1060	7.98	8.20	6.7	6.8
7.	2030	5.26	5.28	5.6	5.9
8.	3050	3.88	3.82	4.5	4.6
9.	4030	3.09	3.11	3.8	3.9
10.	5040	2.56	2.56	3.3	3.3

Output Snap:


Maximum Power Transfer Theorem

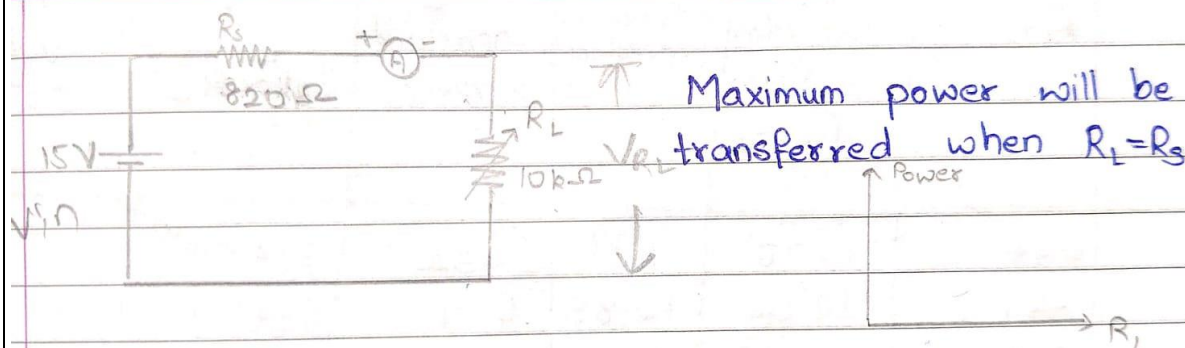

Observation Table:

$R_L (\Omega)$	Current (mA)		V_L across R_L	$P = \frac{V_L^2}{R_L}$	
	Theoretical $I_{th} = \frac{V_{in}}{R_s + R_L}$	Practical		Theoretical $I_{th}^2 \times R_L$	Practical
238	14.78	14.68	3.32	5.2×10^4	4.6×10^4
365	12.66	12.85	4.77	5.8×10^4	6.2×10^4
551	10.89	11.08	6.10	6.6×10^4	6.6×10^4
700	9.87	9.80	6.92	6.81×10^4	6.8×10^4
815	9.17	9.25	7.50	6.85×10^4	6.9×10^4
1060	7.98	8.20	8.56	6.7×10^4	6.8×10^4
2030	5.26	5.28	11.02	5.6×10^4	5.9×10^4
3050	3.88	3.82	11.93	4.5×10^4	4.6×10^4
4030	3.09	3.11	12.59	3.8×10^4	3.9×10^4
5040	2.56	2.56	12.91	3.3×10^4	3.3×10^4

Graph:

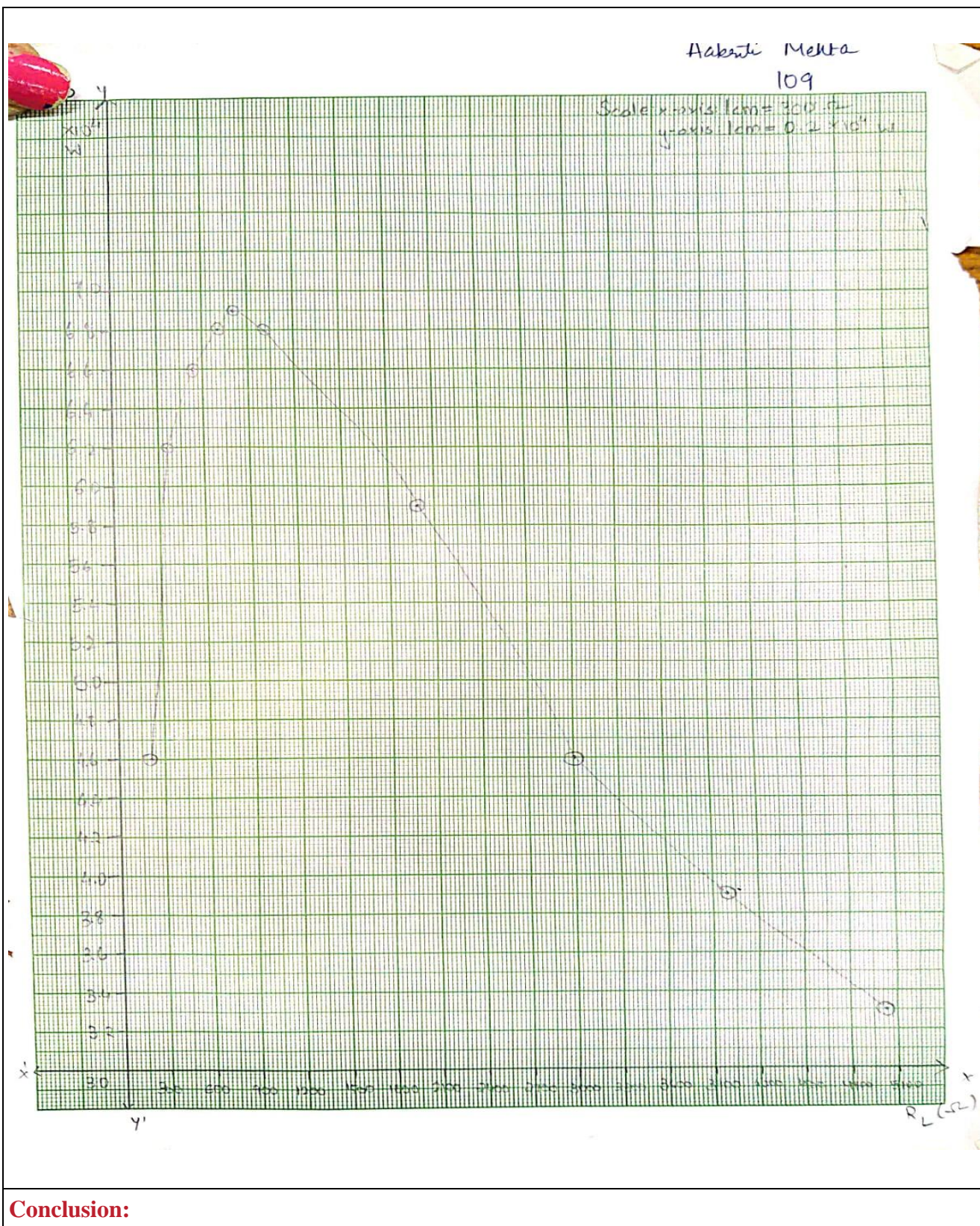



By this experiment we get to know about the maximum power transfer in D.C. circuit.

Signature of faculty in-charge with Date: