



Course Name:	Elements of Electrical and Electronics Engineering	Semester:	I/II
Date of Performance:	27/12/22	Batch No:	C2-2
Faculty Name:	Jyoti Varavedkar	Roll No:	16010122109
Faculty Sign & Date:		Grade/Marks:	/ 25

Experiment No: 10

Title: Inverting and Non-inverting amplifier using OPAMP

Aim and Objective of the Experiment:


- To understand inverting configuration of OPAMP
- To understand Non-inverting configuration of OPAMP
- the concept of negative feedback and closed loop configuration of OPAMP.
- To understand gain of inverting and non-inverting OPAMP

COs to be achieved:

CO5: Understand operational amplifier and its applications

Circuit Diagram/ Block Diagram:

Pin diagram of IC 741

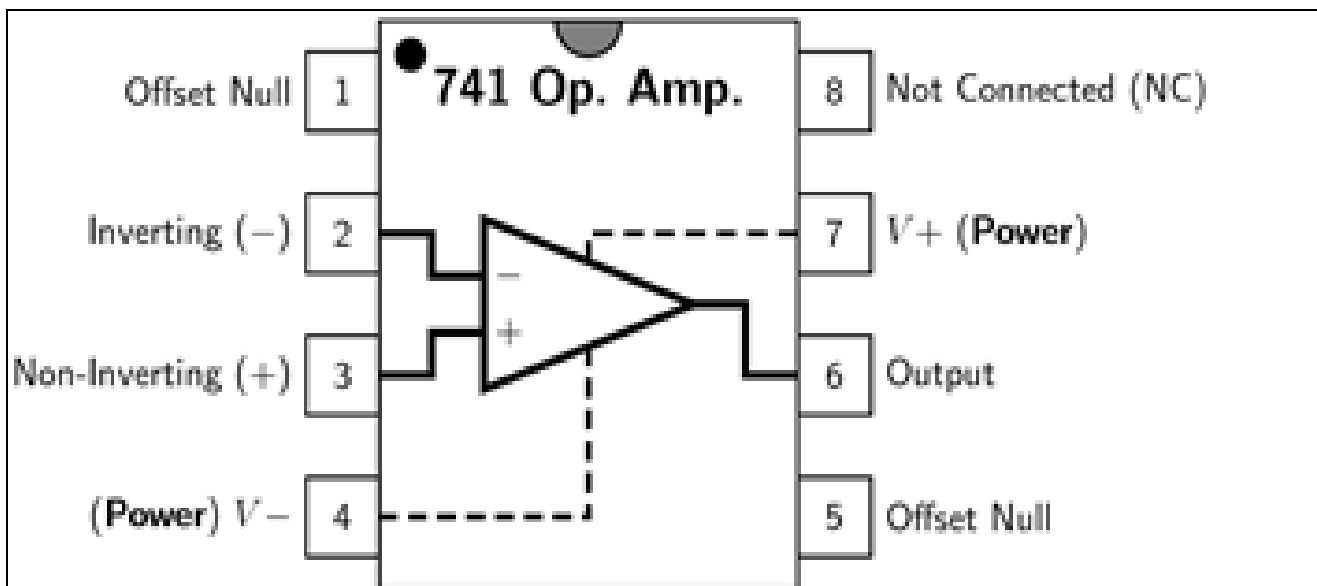

Procedure

1. Click on following link for Virtual lab experiment.

<http://vlabs.iitkgp.ac.in/be/exp17/index.html#>

2. Go through the theory, solve pre-quiz.
3. Go to simulation and perform the experiment by following the given procedure.
4. Prepare observation table, plot the graph based on observations.
5. Write conclusion based on observations.

Observations:


INSTRUCTION

EXPERIMENTAL TABLE

Resistance: K Ω

Serial No.	Input Voltage V	Output Voltage V	Current mA
1	1	-5.00	0.400
2	2	-10.0	0.800

Inverting Opamp

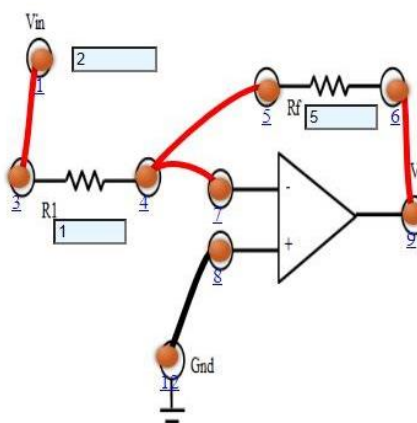

CONTROLS

Input volt : Volt

Resistance (R₁) : Kohms

Resistance (R_f) : Kohms

Add to Table
Plot
Clear

-10.0


0.800

-5

-5

Check connection

Delete all connection

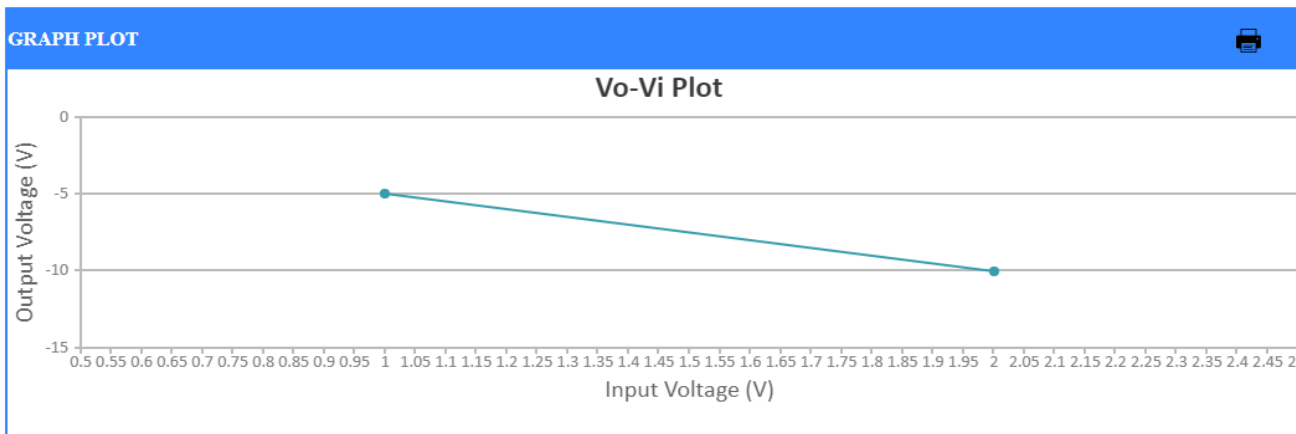


INSTRUCTION

EXPERIMENTAL TABLE

Resistance: K Ω

Serial No.	Input Voltage V	Output Voltage V	Current mA
1	1		NaN
2	2	-4.00	0.500

Inverting Opamp

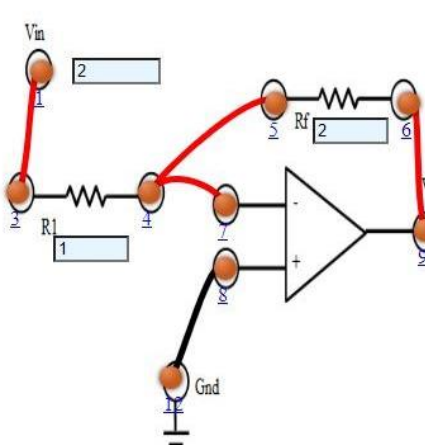

CONTROLS

Input volt : Volt

Resistance (R_1) : Kohms

Resistance (R_f) : Kohms

Add to Table

Plot

Check connection

Clear

Delete all connection

NON - INVERTING :


INSTRUCTION

EXPERIMENTAL TABLE

Resistance: K Ω

Serial No.	Input Voltage V	Output Voltage V	Current mA
1	1	6.00	0.467
2	2	12.0	0.933

Non Inverting Opamp

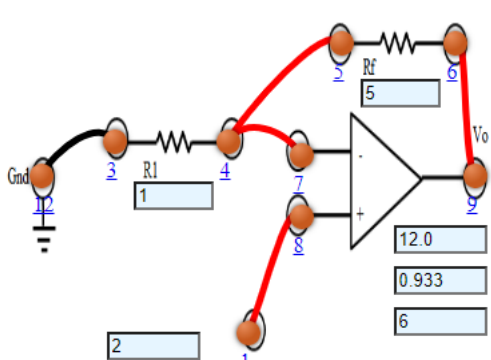

CONTROLS

Input volt : Volt

Resistance (R_1) : Kohms

Resistance (R_f) : Kohms

Add to Table

Plot

Check connection

Clear

Delete all connection

Print It


INSTRUCTION

EXPERIMENTAL TABLE

Resistance: K Ω

Serial No.	Input Voltage V	Output Voltage V	Current mA
1	1	4.00	0.385
2	2	8.00	0.769

Non Inverting Opamp

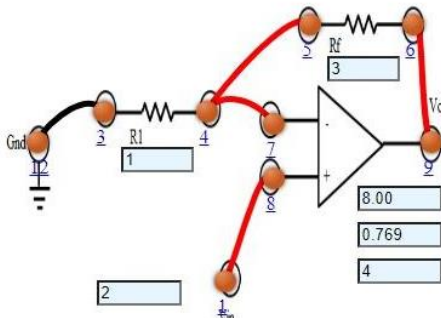

CONTROLS


Input volt : Volt

Resistance (R₁) : Kohms

Resistance (R_f) : Kohms

Add to Table
Plot
Clear

Check connection
Delete all connection

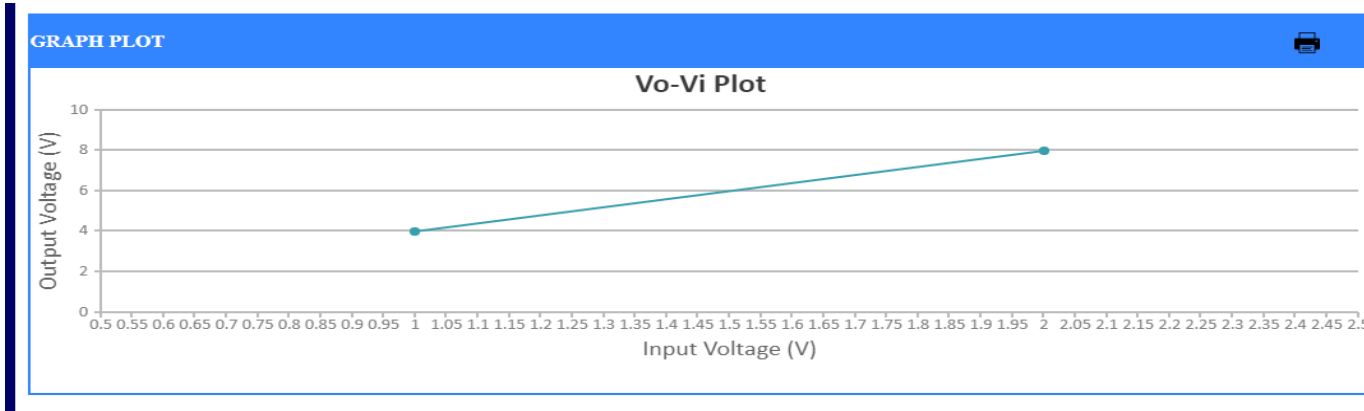

Conclusion:

Thus, we learnt the working of OPAMP in inverting and non-inverting configuration.

Signature of faculty in-charge with Date: