



Course Name:	Elements of Electrical and Electronics Engineering	Semester:	I
Date of Performance:	15 / 11 / 2022	Batch No:	C2-2
Faculty Name:	Jyoti Varavedkar	Roll No:	16010122109
Faculty Sign & Date:		Grade/Marks:	/ 25

Experiment No: 4

Title: Thevenin's Theorem & Norton's Theorem.

Aim and Objective of the Experiment:


- To Verify for Thevenin Theorem for the circuit
- To Verify Norton Theorem for the Circuit.

COs to be achieved:


CO1: Analyze resistive networks excited by DC sources using various network theorems.
.


Circuit Diagram/ Block Diagram:

Circuit Diagram:

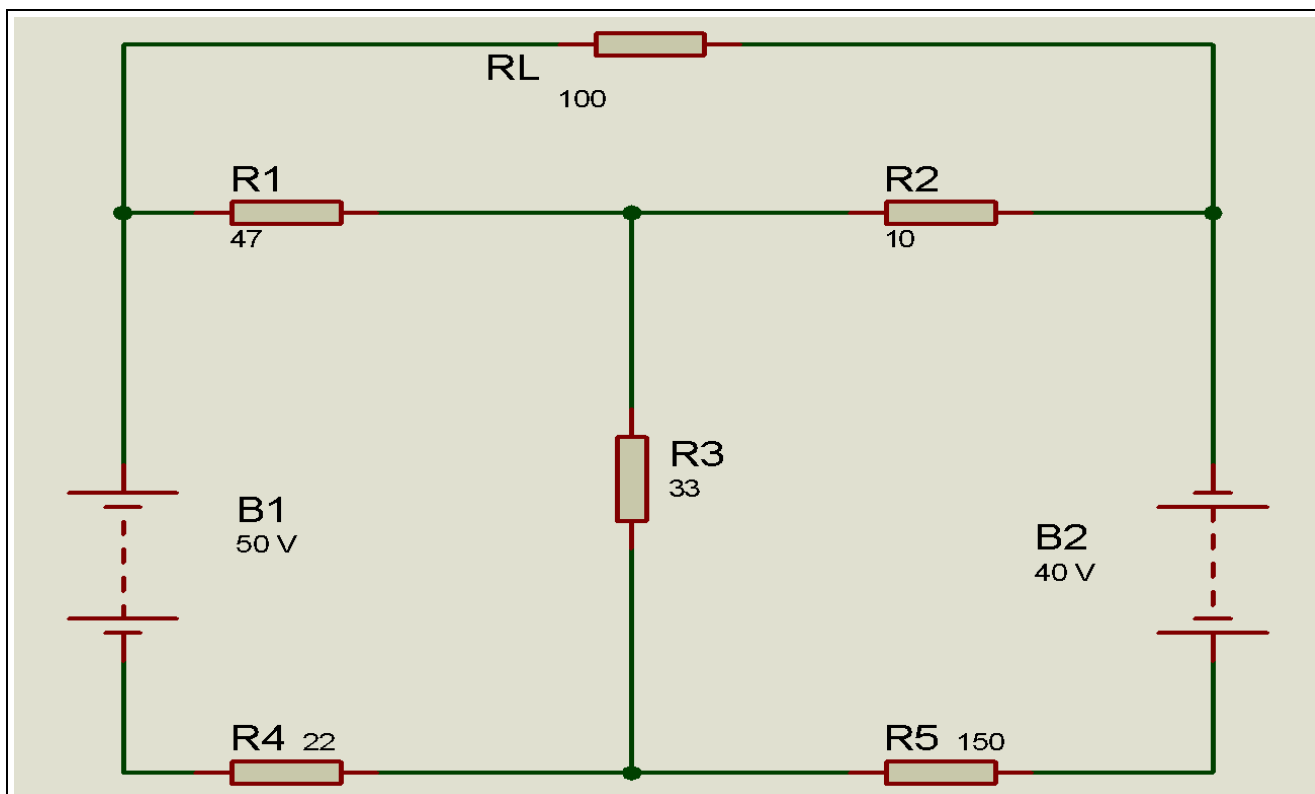


Task 1: Circuit Diagram to measure R_{TH}/R_N :

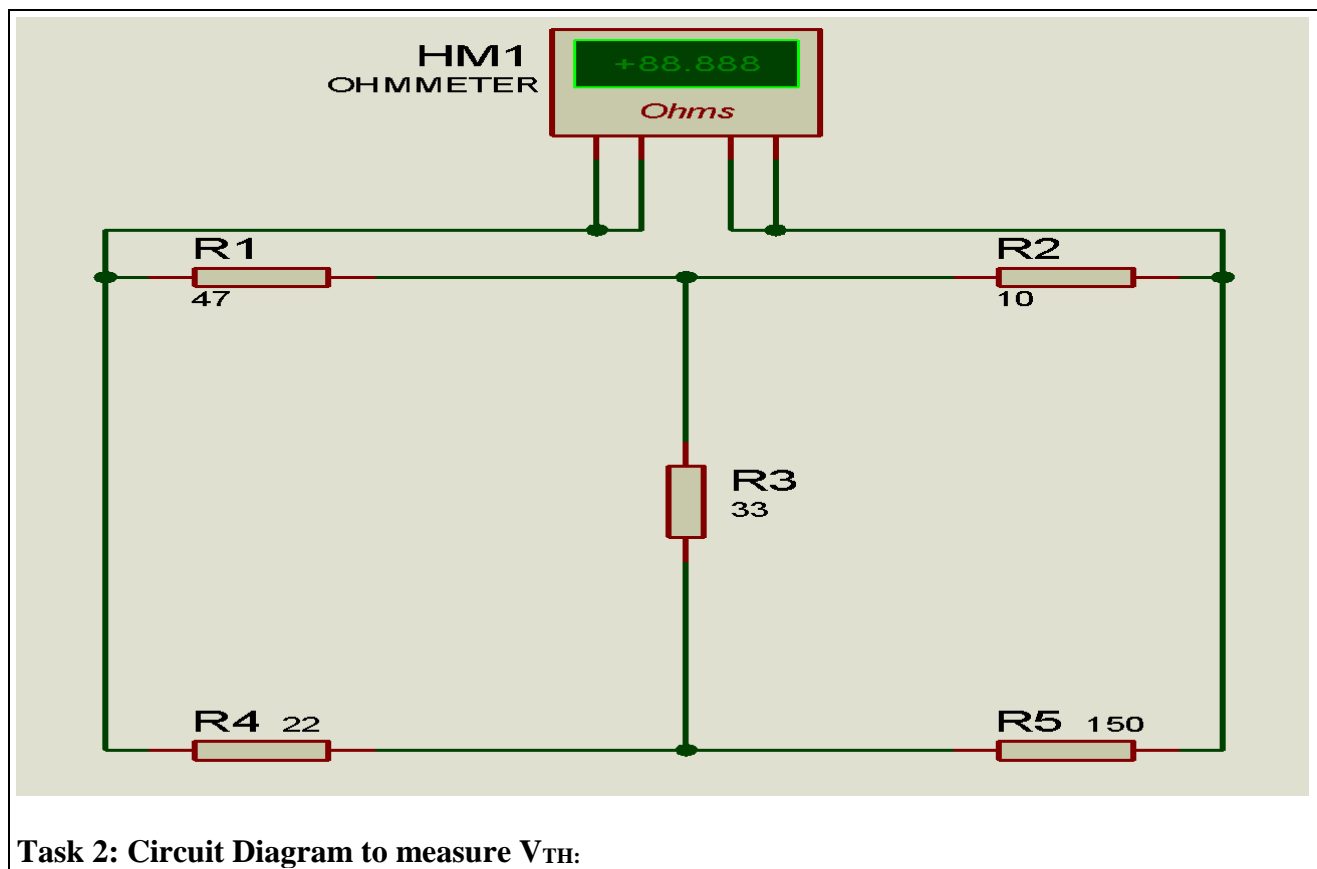

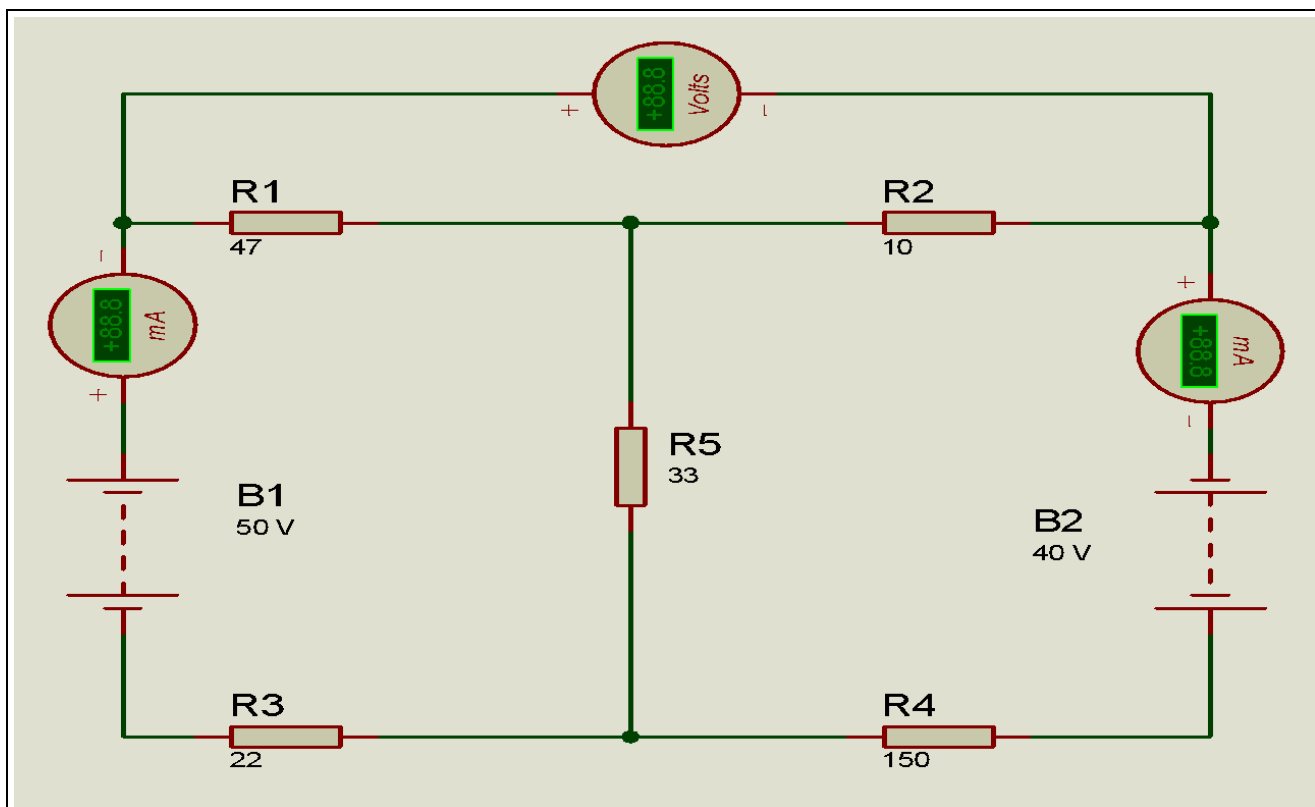

Task 3: Circuit Diagram to measure Isc:

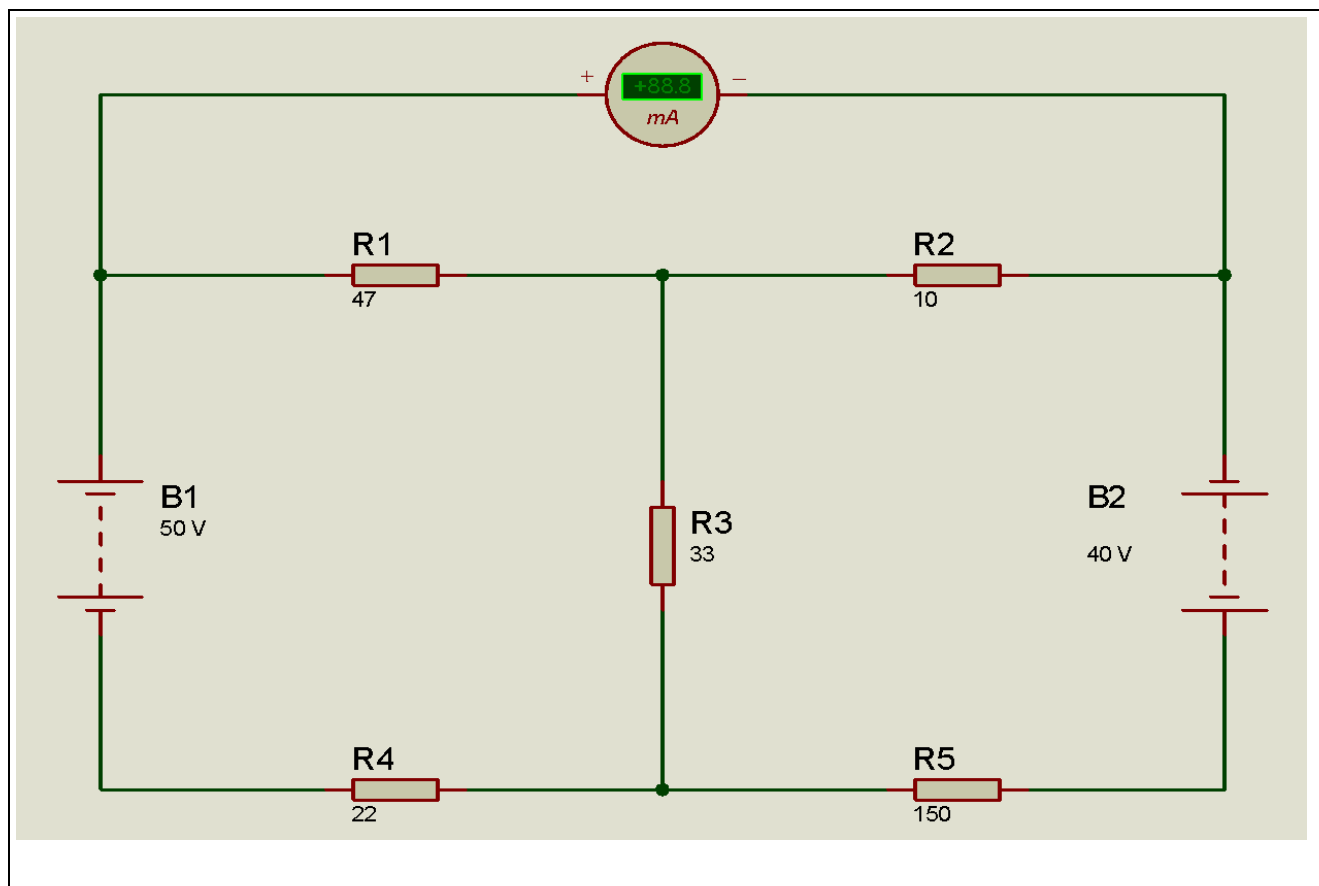

Stepwise-Procedure:

Thevenin's Theorem:

1. Connect the circuit as shown in the circuit diagram.
2. Set V_1 , V_2 and measure open circuit voltage V_{Th} across load terminals A and B.
3. Replace all voltage sources by Short circuit and measure R_{Th} across terminals A and B as per the circuit diagram shown in the figure.
4. Draw Thevenin's equivalent circuit and determine the value of load current from it.
5. Verify the results theoretically.


Norton's Theorem:

1. Connect the circuit as shown in the circuit diagram.
2. Set the voltages V_1 , V_2
3. Remove the load resistance and measure the short circuit current I_{SC} through A and B terminals.
4. Replace all the voltage sources by Short circuit and measure R_{Th} across terminals A and B as per the circuit diagram shown in the figure.
5. Draw Norton's equivalent circuit and determine the value of load current.
6. Verify the results theoretically

Sample Calculations:

Page No. _____
 Date _____

Thevenin's Theorem & Norton's Theorem

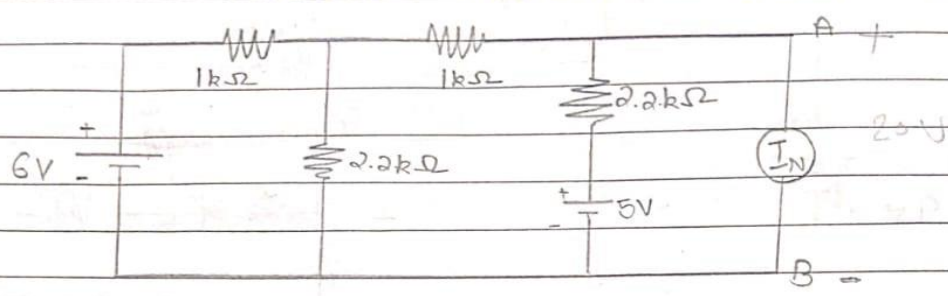


- 1) Measurement of V_{th} :
 - Open ckt R_L and measure V_{th} betⁿ A & B.
- 2) Measurement of R_{th} :
 - Remove R_L , short ckt both supplies and calculate R_{th} theoretically & also measure practically.
- 3) Measurement of I_N for Norton's Theorem :
 - Remove R_L and short ckt betⁿ A and B and calculate I_N theoretically value. Practically measure I_N by connecting multimeter in current mode in A & B.

- Observation Table:

	V_{th}	R_{th}	I_N
Theoretical value	4.95V	0.955kΩ	4.71mA
Practical value	4.85V	0.93kΩ	4.82mA

Resultant ckt for
 R_{th}

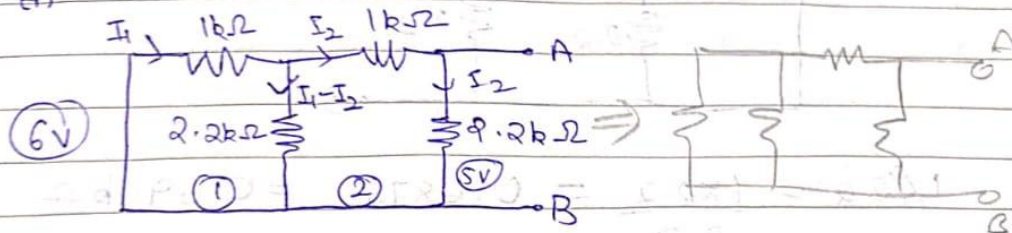

mesh ①

mesh ②

$$6 - 1I_1 - 2.2(I_1 - I_2) = 0 \quad \text{--- mesh ①}$$

$$3.2I_1 - 2.2I_2 = 6 \quad \text{--- mesh ②}$$

$$3.2I_1 - 2.2I_2 = 6$$

$$16I_1 - 11I_2 = 30$$

$$176I_1 - 121I_2 = 330 \quad \text{①}$$

$$176I_1 - 121I_2 = 330$$

$$176I_1 - 432I_2 = 400$$

$$- \quad + \quad -$$

$$311I_2 = 70$$

$$I_2 = \frac{70}{311} = 0.225 \text{ A}$$

$$311$$

$$16I_1 - 770 = 30$$

$$311$$

$$16I_1 = \frac{9330 + 770}{311} = \frac{10100}{311} \quad \text{--- ① dom}$$

$$I_1 = 2.03 \text{ A}$$

$$I_1 = 2.03 \text{ A}$$

$$I_2 = 0.225 \text{ A}$$

$$I_2 = 0.225 \text{ A}$$


$$I = 2.25 \text{ A}$$

$$V_{th} = IR$$

$$V_{th} = 2.25 \times 2.2$$

$$V_{th} = 4.95 \text{ V}$$

Page No. _____
 Date ____/____/____

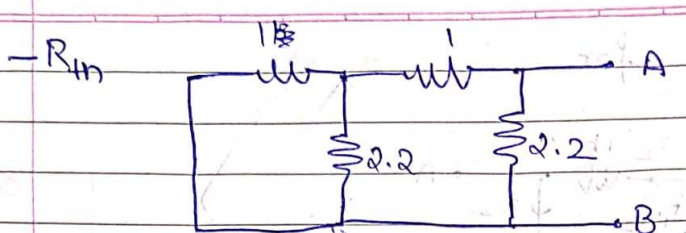


$$\frac{1}{\frac{1}{2.2} + \frac{1}{1 + 2.2}} = \frac{1 \times 2.2}{3.2} = 0.6875 = 0.69 \text{ k}\Omega$$

$$0.69 + 1 = 1.69 \text{ k}\Omega$$

$$\frac{1.69}{1 + 2.2} = \frac{1.69 \times 2.2}{3.89} = 0.9557 \text{ k}\Omega = 955.7 \Omega$$

$$R_{th} = 955.7 \Omega$$

- I_N For calculation of I_N


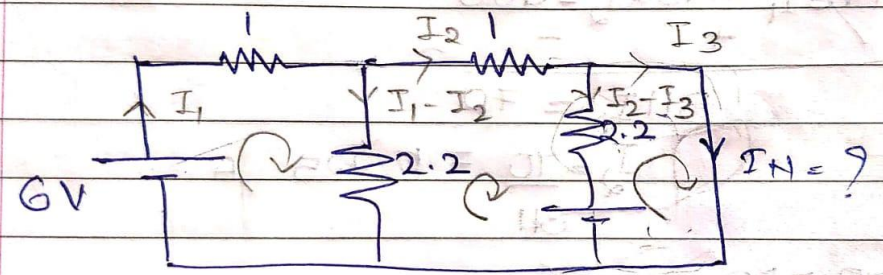


$I_N = 4.71 \text{ mA}$

Observation Table:

	V_{TH} In volts	R_{TH} / R_N In Ω	I_N in mA
Theoretical value	4.95	955	4.71
Practical value	4.85	950	4.82

Screenshot of Output (Thevenin's and Norton's method):

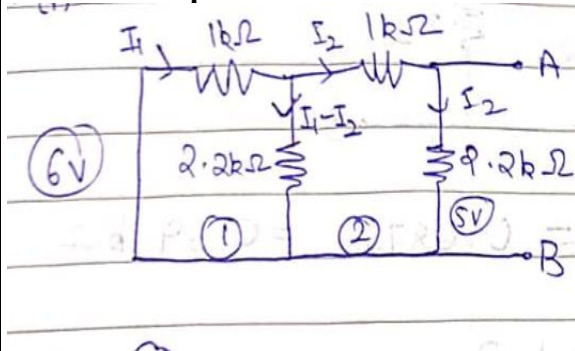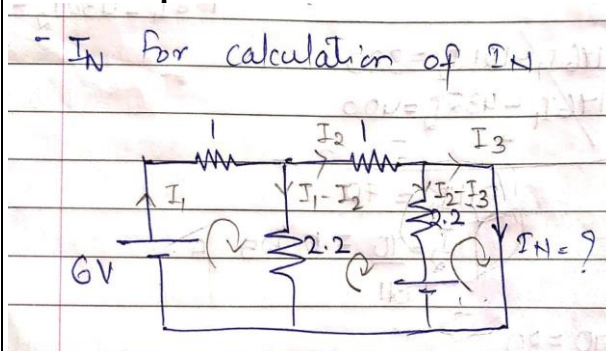Thevenin's equivalent circuit:

Norton's equivalent circuit:

 R_{TH}/R_N :
950 ohms
O/P for I_N :
4.82 mA
Conclusion:

By this experiment we get to know about the Thevenin Theorem and Norton Theorem for the circuit.



SOMAIYA
VIDYAVIHAR UNIVERSITY

K J Somaiya College of Engineering

K. J. Somaiya College of Engineering, Mumbai-77

(A Constituent College of Somaiya Vidyavihar University)

Department of Sciences and Humanities



Signature of faculty in-charge with Date: